

Science lesson wb:15.09.25

All: To identify components of a circuit.

All: To build and test simple circuits.

Y4: Explain what a complete and incomplete circuit is.



